

STAIRCASE WIRING

Aim :

To develop and test the staircase wiring using protens.

APPARATUS REQUIRED :

Laptop with protens software.


THEORY :

Staircase wiring is a common multiple way switching or two way switching connection. It involves wiring for one light with two switches. In this set up is controlled by two switches located at different position. It allows the user to operate the load from separate position above or below the staircase from ~~inside~~ or outside of room or two way led switch.

PROCEDURE :

Drag the required components from the protens library.

CIRCUIT DIAGRAM :

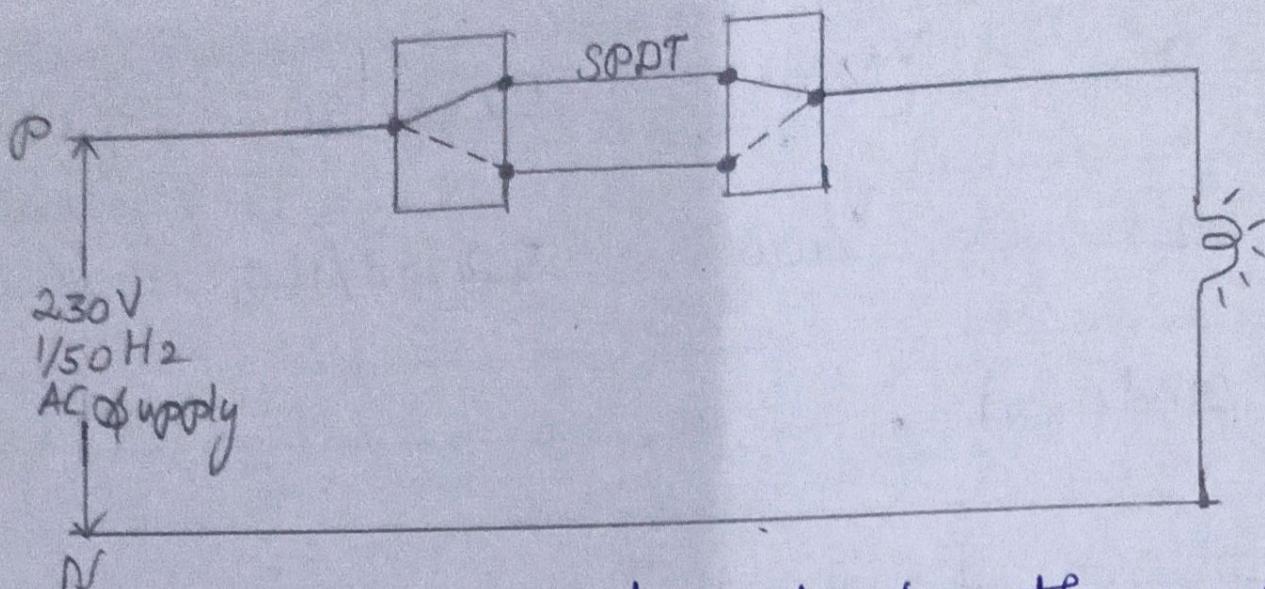


NODE	S ₁	S ₂	LAMP
1	ON	ON	ON
2	ON	OFF	OFF
3	OFF	ON	OFF
4	OFF	OFF	ON



COMPONENTS	PROTEUS	SPECIFICATION
AC Supply	Vsin	Amplitude = 230V
Two-way switch	SPDT	Frequency = 50Hz
Lamp	Animated	230V

CROSS

CONNECTION :


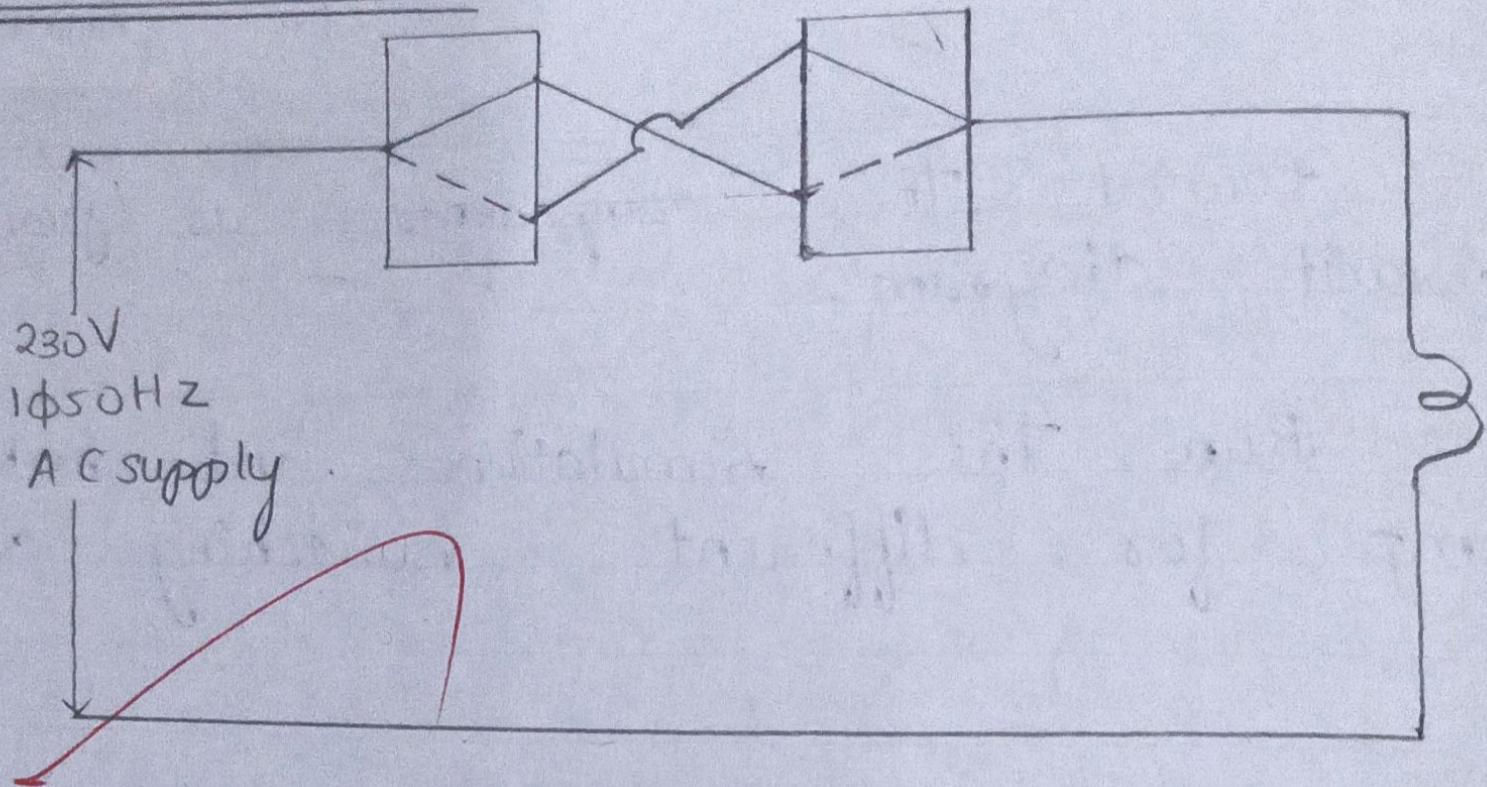


NODE	S_1	S_2	LAMP
1	ON	ON	OFF
2	ON	OFF	ON
3	OFF	ON	ON
4	OFF	OFF	OFF

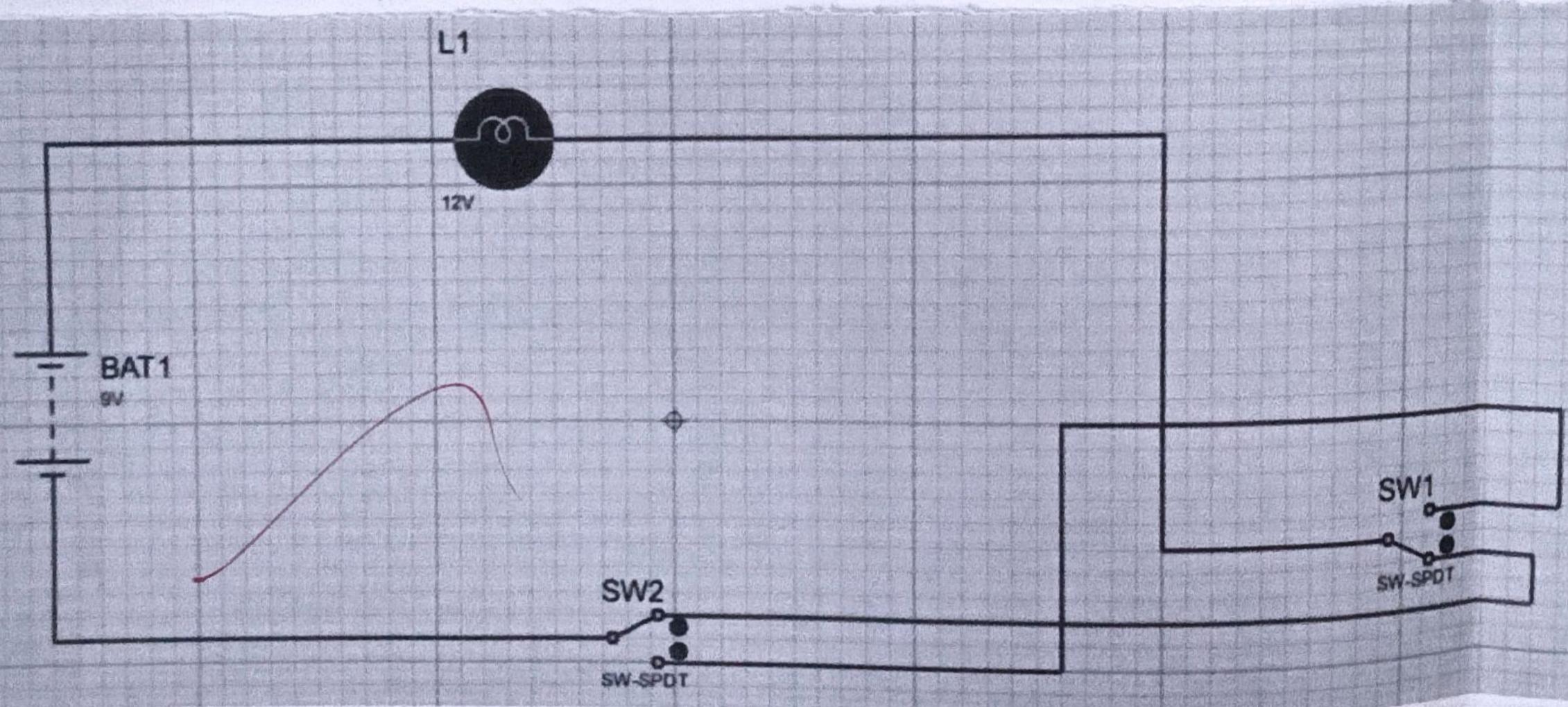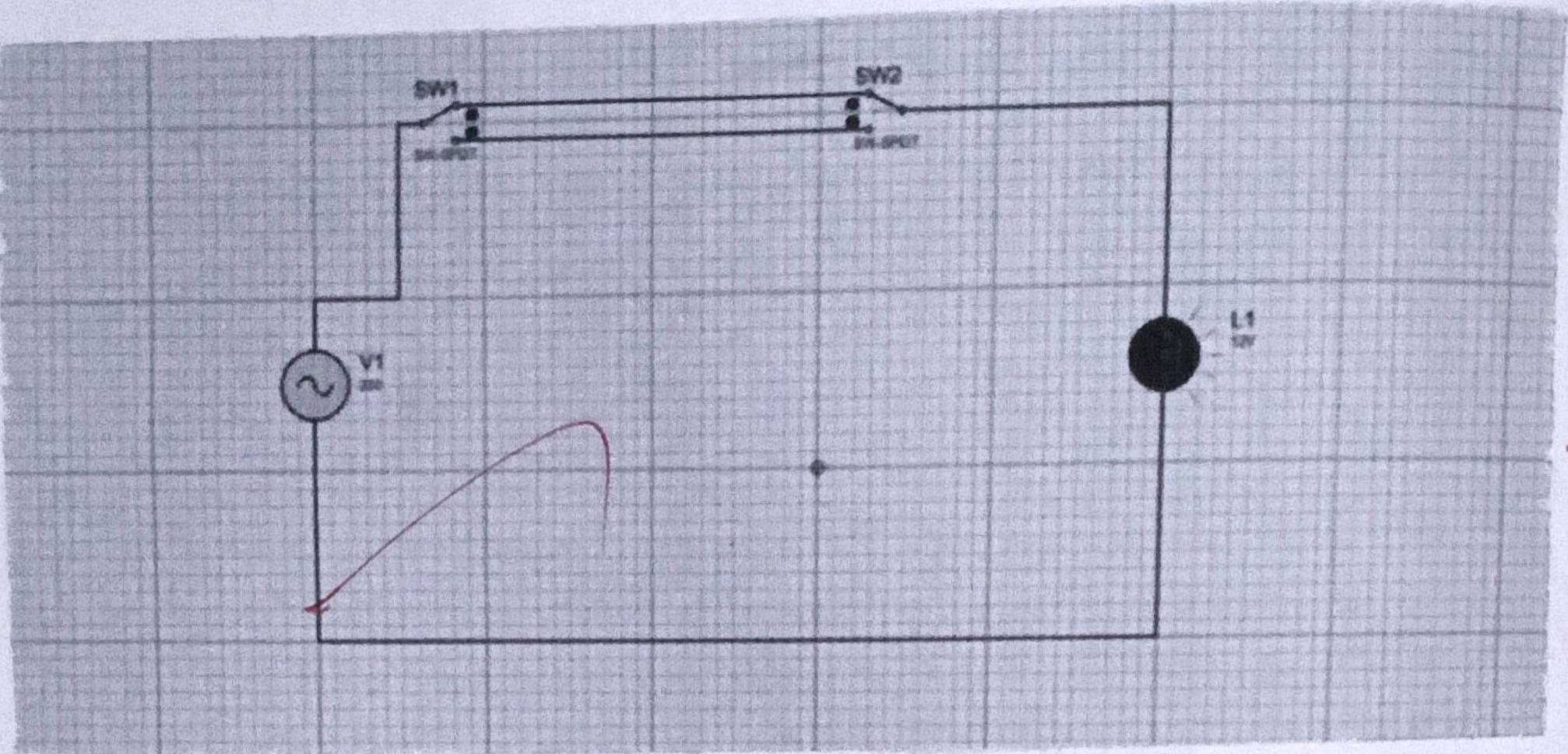

connected the components as per the circuit diagram.

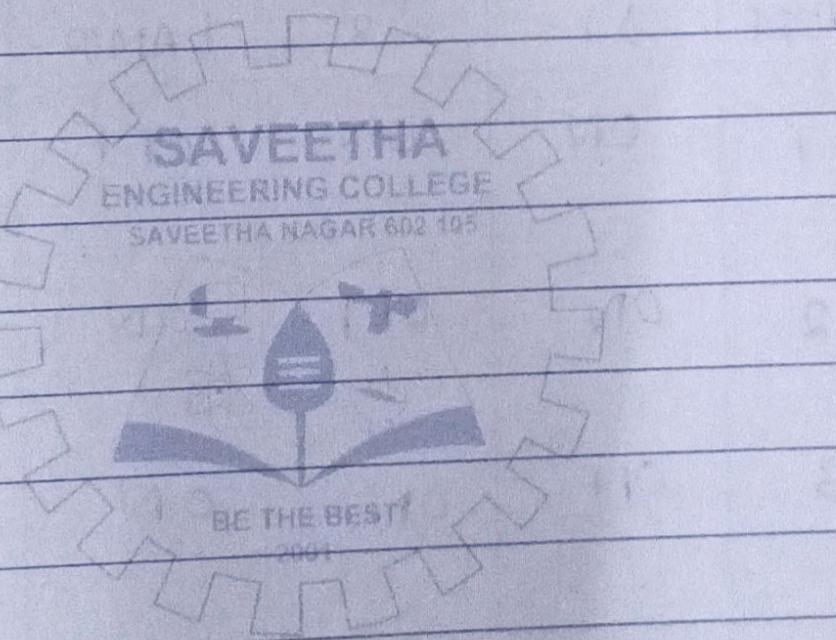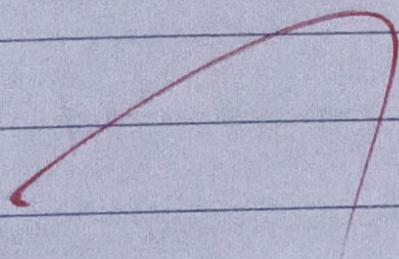Run the simulation and check the lamp for different switching conditions.



~~RESULT:~~

Thus the staircase wiring connections were developed and tested successfully.